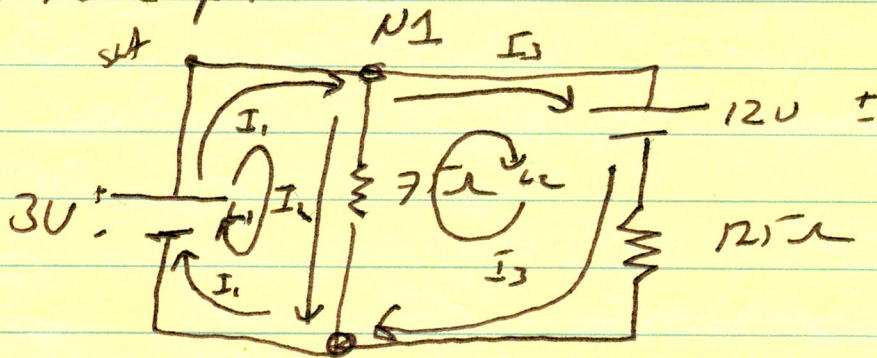


- Need to use with multiple batteries
- Use when can't solve for Equivalent resistance

\* Make so student  
see videos on  
about  
3/5/17

## Kirchoff's Loop Rule




- Identify the nodes ( $N_1$  &  $N_2$ ) conventional current = + flow
  - Identify Direction of Current - Direction of the current is arbitrary  
If you get a positive Ans. for the current, you chose the right direction  
If you get a negative Ans. for the current, the current is flowing in the opposite direction
  - Need to make a Voltage loop (Arbitrary Also)
  - Apply current rule into the Junctions  $\sum I = 0$   
(same as cons. of Charge)  
Sum of Current entering Node is equal to sum of current leaving node  
~~for~~  $I_{in} = +$        $Out = -$
- $N_1$ :  $I_1 - I_2 - I_3 = 0$   
 $I_1 = I_2 + I_3$
- $N_2$ :  $I_2 + I_3 - I_1 = 0$   
 $I_1 = I_2 + I_3$
- Same Eqn only need 1

$$v = IR$$

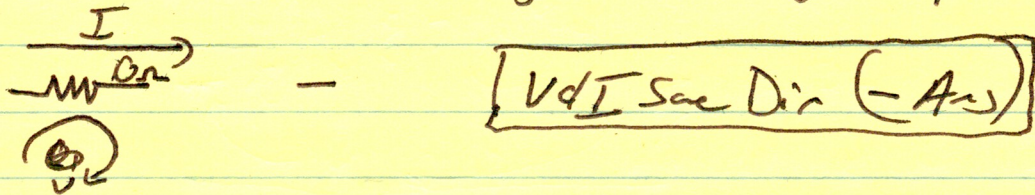5. Voltage Rule (Apply to Each loop) & Ohm's Law  
 Sum of the Voltages across elements in the loop is equal to zero  $\sum V = 0$


$v = IR$  \*  
 $-10I$   
 pot. Dec  
 low to high

Voltage with current you get a Voltage Drop (-)




Ex


+5V  
 pot. Gain

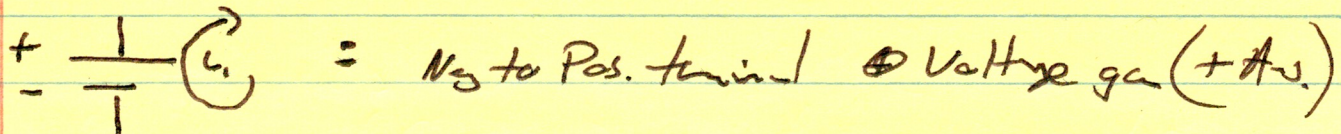

-5V  
 pot. Dec

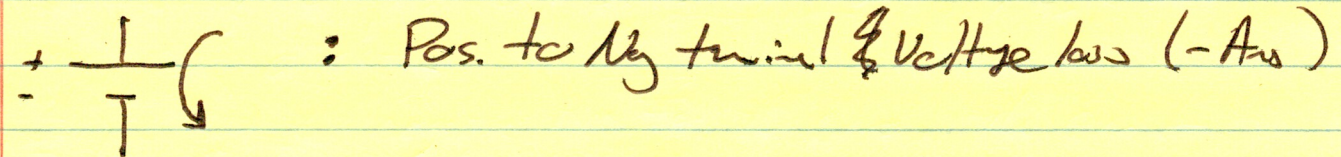

$v = IR$   
 $+10I$   
 on high

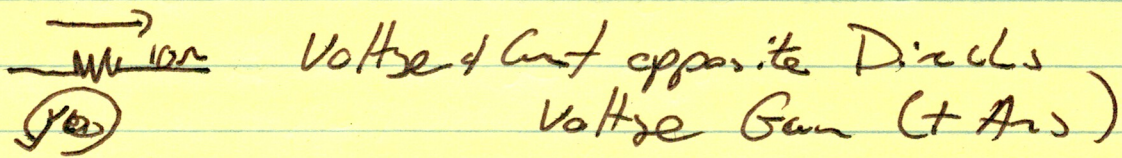

$$U = qV$$

$$v = IR$$

$$L_1: -75I_2 + 3V = 0$$

$$\textcircled{B} -75I_2 + 3 = 0$$

~~$$75I_2 = 3$$~~

$$L_2: -12V + 125I_3 + 75I_2 = 0$$

$$-12 + 125I_3 + 75I_2 = 0$$

~~$$125I_3 + 75I_2 = 12$$~~

⑥ Solve the 3 Eqs


$$N_1: I_1 = I_2 + I_3$$

$$L_1: -75I_2 + 3 = 0$$

$$L_2: ~~125I_3 + 75~~ -12 + 125I_3 + 75I_2 = 0$$

$$L_1: \frac{3}{75} = \frac{75I_2}{75}$$

$$I_2 = 0.04A$$

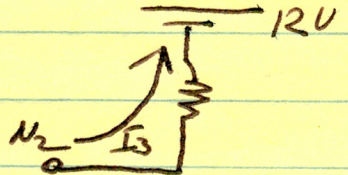

$$L_2: -12 - 125I_3 + 75I_2 = 0$$

$$-12 - 125I_3 + 75(0.04A) = 0$$

$$-12 - 125I_3 + 3 = 0$$

$$I_3 = \frac{12-3}{-125} = -0.072A$$

$$I_3 = -0.072A$$

$$I_3 = -0.072A$$

- Magnitude of current is 0.072A


- We chose wrong dir for I3

- Doesn't mean current is 0

$$N_1: I_1 = I_2 + I_3$$



$$0.04A - 0.072A$$

$$I_1 = -0.032A$$

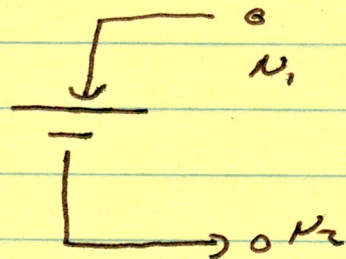
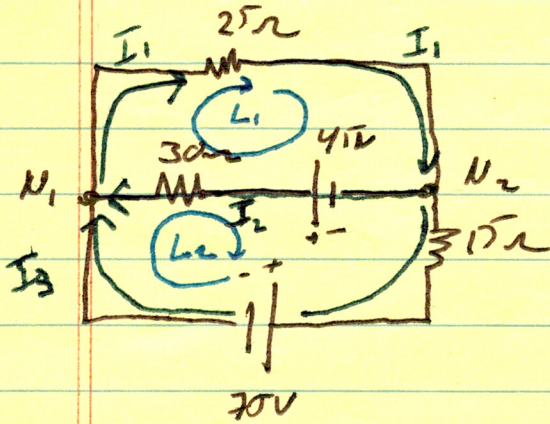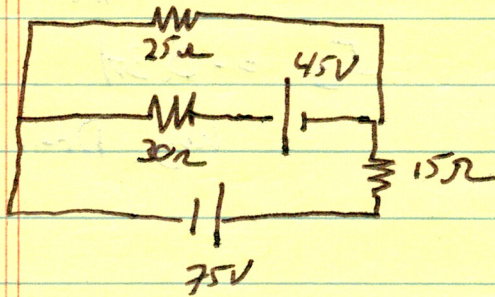
## Ex. #2

Find the current & Direction of current on the 3 branches of the circuit:



- ① Id Nodes
- ② Id Dir. of current for each Branch
- ③ Current Rule @ Nodes

Sum of current Enter = Sum of current Leave

$$N_1: I_2 + I_3 - I_1 = 0$$

$$I_1 = I_2 + I_3$$

$$N_2: I_1 - I_2 - I_3 = 0$$

$$I_1 = I_2 + I_3$$

Int. Need  
see N.

④ Voltage loops w/ dir's  $V = IR$

$$L_1: -25I_1 + 45 - 30I_2 = 0$$

$$L_2: 30I_2 - 45 - 15I_3 - 75 = 0$$

$$L_1 \text{ solve for } I_1: -25I_1 = -45 + 30I_2$$

$$I_1 = 1.8 - 1.2I_2$$

$$L_2: 30I_2 - 45 - 15I_3 - 75 = 0$$

$$-15I_3 = 120 - 30I_2$$

$$I_3 = -8 + 2I_2$$

$$N_1: I_1 = I_2 + I_3 \text{ or } I_2 = I_1 - I_3$$

$$I_2 = 1.8 - 1.2I_2 - (-8 + 2I_2)$$

$$1.8 - 1.2I_2 + 8 - 2I_2$$



$$I_2 = 9.8 - 3.2I_2$$

$$4.2I_2 = 9.8$$

$$\boxed{I_2 = 2.3A}$$
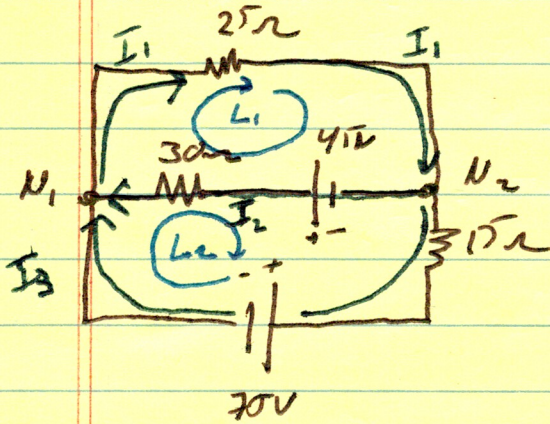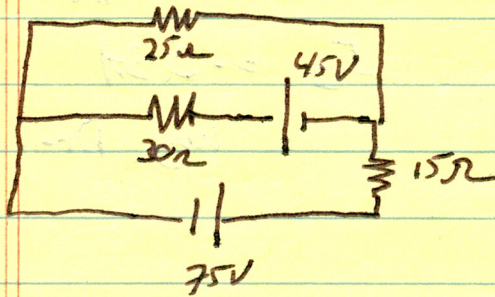
## Ex. #2

Find the current & Direction of current on the 3 branches of the circuit:



- ① Id Nodes
- ② Id Dir. of current for each Branch
- ③ Current Rule @ Nodes

Sum of current Enter = Sum of current Leave

$$N_1: I_2 + I_3 - I_1 = 0$$

$$I_1 = I_2 + I_3$$

$$N_2: I_1 - I_2 - I_3 = 0$$

$$I_1 = I_2 + I_3$$

Int. Need  
see N.

④ Voltage loops w/ dir's  $V = IR$

Start at  $N_1$

$$L_1: -25I_1 + 45 - 30I_2 = 0$$

$$L_2: 30I_2 - 45 - 15I_3 - 75 = 0$$

$$L_1 \text{ solve for } I_1: -25I_1 = -45 + 30I_2$$

$$I_1 = 1.8 - 1.2I_2$$

$$L_2: 30I_2 - 45 - 15I_3 - 75 = 0$$

$$-15I_3 = 120 - 30I_2$$

$$I_3 = -8 + 2I_2$$

$$N_1: I_1 = I_2 + I_3 \text{ or } I_2 = I_1 - I_3$$

$$I_2 = 1.8 - 1.2I_2 - (-8 + 2I_2)$$

$$1.8 - 1.2I_2 + 8 - 2I_2$$

$$I_2 = 9.8 - 3.2I_2$$

$$4.2I_2 = 9.8$$

$$\boxed{I_2 = 2.3A}$$