

Questions

- 1 The diagram at the right represents a segment of a circuit. The current in wire X may be

(1) 1 ampere
(2) 2 amperes
(3) 3 amperes
(4) 4 amperes

- 2 In the diagram shown, how many amperes is the reading on ammeter A?

(1) 5 amperes
(2) 2 amperes
(3) 3 amperes
(4) 7 amperes

- 3 If the potential difference between points A and B in the electric circuit shown is 10 volts, what is the voltage between points A and C?

(1) 5 volts
(2) 10 volts
(3) 20 volts
(4) 30 volts

- 4 If 4 joules of work are required to move 2 coulombs of charge through a 6-ohm resistor, the potential difference across the resistor is

(1) 1 volt
(2) 2 volts
(3) 6 volts
(4) 8 volts

- 5 In the circuit represented, which switch or switches must be closed to produce a current in conductor AB?

(1) 1 and 4, only
(2) 2 and 3, only
(3) 1, 2, and 3
(4) 4, only

- Which quantity must be the same for each component in a series circuit?

(1) voltage
(2) power
(3) resistance
(4) current

the diagram?

(1) 1 amp
(2) 2 amp
(3) 3 amp
(4) 4 amp

- The diagram represents a circuit with two resistors in series. If the total resistance of R_1 and R_2 is 24 ohms, the resistance of R_2 is

(1) 1.0 ohm
(2) 0.50 ohm
(3) 100 ohm
(4) 1.0 ohm

- A 20-ohm resistor and a 20-ohm resistor are connected in parallel to a constant voltage source. If the current through the 10-ohm resistor is 4.0 amperes, then the current through the 20-ohm resistor is

(1) 1 ampere
(2) 2 amperes
(3) 8 amperes
(4) 4 amperes


- As the number of resistors connected in parallel to a constant voltage source is increased, the potential difference across each resistor

(1) decreases
(2) increases
(3) remains the same

Series and Parallel Circuits and Kirchhoff's Laws

- 11 Compared to the current in the 20. ohm resistance in the circuit diagram shown, the current in the 5.0 ohm resistor is

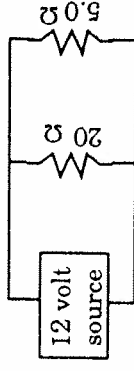
(1) one-half as great
(2) one-fourth as great
(3) the same
(4) four times as great



- Base your answers to questions 12 through 15 on the diagram in which the source voltage is 26 volts.

$$V = IR$$

$$I_T = 2A$$

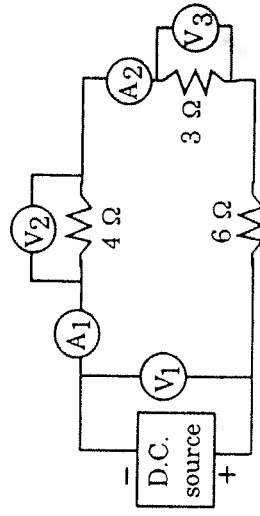

- 12 What is the reading of voltmeter V_2 ?

(1) 52 volts
(2) 26 volts
(3) 13 volts
(4) 8 volts

- 13 What is the total resistance of the circuit?

(1) $\frac{3}{4}$ ohm
(2) $\frac{4}{3}$ ohm
(3) 10 ohm
(4) 13 ohm


- 14 The reading of ammeter A_1 is

(1) 6 amperes
(2) 2 amperes
(3) 3 amperes
(4) 52 amperes

- 15 If additional resistances are added in series and the applied voltage is kept constant, the reading of voltmeter V_3 will

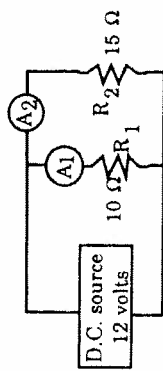(1) decrease
(2) increase
(3) remain the same
(4) increase

- Base your answers to questions 16 through 20 on the diagram below which represents an electrical circuit.



- 16 The equivalent resistance of the circuit is

(1) 25 ohm
(2) 6.0 ohm
(3) 5.0 ohm
(4) 0.17 ohm

- 17 The potential difference across R_2 is

(1) 1.0 V
(2) 2.0 V
(3) 10 V
(4) 12 V

- 18 The magnitude of the current in ammeter A_1 is

(1) 120 A
(2) 2.0 A
(3) 1.2 A
(4) 0.83 A

- 19 Compared to the current in A_1 , the current in A_2 is

(1) less
(2) greater
(3) the same
(4) more


- 20 If another resistor were added to the circuit in parallel, the equivalent resistance of the circuit would

(1) decrease
(2) increase
(3) remain the same
(4) increase

1 Which combination of current and electromotive force (emf) would use energy at the greatest rate? - Power

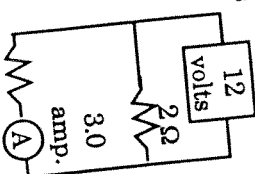- (1) 10 amperes at 110 volts
(2) 8 amperes at 110 volts
(3) 3 amperes at 220 volts
(4) 5 amperes at 110 volts

2 Two resistors are connected in parallel to a 12-volt battery as shown in the diagram. If the current in resistance R is 3.0 amperes, the rate at which R consumes electrical energy is



- (1) 1.1×10^2 watts
(2) 36 watts
(3) 24 watts
(4) 4.0 watts

3 The potential difference across a 100.-ohm resistor is 4.0 volts. What is the power dissipated in the resistor?

- (1) 0.16 watt
(2) 25 watts
(3) 4.0×10^2 watts
(4) 4.0 watts

4 An electrical heater raises the temperature of a measured quantity of water. Six thousand joules of energy is absorbed by the water from the heater in 30.0 seconds. What is the minimum power rating of the heater?

- (1) 5.00×10^2 W
(2) 2.00×10^2 W
(3) 2.00×10^3 W
(4) 1.80×10^5 W

5 What is the current in a 1,200-watt heater operating on 120 volts?

- (1) 0.10 ampere
(2) 5.0 amperes
(3) 10. amperes
(4) 20. amperes

6 A 10-volt potential difference maintains a 2-ampere current in a resistor. The total energy expended by this resistor in 5 seconds is

- (1) 10 J
(2) 20 J
(3) 50 J
(4) 100 J


7 How long must a 100-watt light bulb be used in order to dissipate 1,000 joules of electrical energy?

- (1) 10 sec
(2) 100 sec
(3) 1,000 sec
(4) 1000,000 sec

8 As the resistance of a lamp operated at a constant voltage increases, the power used by the lamp

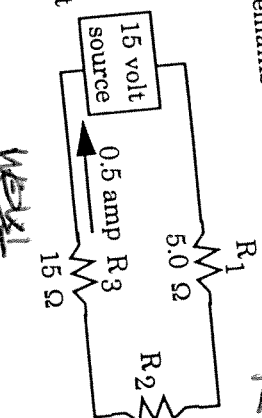- (1) decreases
(2) increases
(3) remains the same
(4) 1000,000 sec

Base your answers to questions 9 through 13 on the diagram below which shows resistors connected to a 15-volt source.



WELL

$V = IR$
 $I = \frac{V}{R}$
 R_T

$W = VIT$

9 The equivalent resistance of the circuit is

- (1) 10 ohms
(2) 20 ohms
(3) 30 ohms
(4) 40 ohms

10 The potential difference across R_2 is

- (1) 2.5 volts
(2) 5.0 volts
(3) 7.5 volts
(4) 10 volts

11 The total power developed in the circuit is


- (1) 2.5 watts
(2) 5.0 watts
(3) 7.5 watts
(4) 10 watts

12 If resistor R_3 is removed and replaced by a resistor of lower value, the resistance of the circuit will

- (1) decrease
(2) increase
(3) remain the same

13 Compared to the heat developed in resistor R_1 , the heat developed in resistor R_3 is

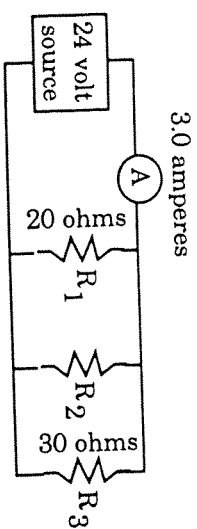- (1) one-third as great
(2) two times as great
(3) three times as great
(4) one-fourth as great



14 The equivalent resistance in the circuit is

- (1) 0.13 ohms
(2) 8.0 ohms
(3) 58 ohms
(4) 72 ohms

15 The current in R_1 is

- (1) 0.83 amperes
(2) 1.5 amperes
(3) 3.0 amperes
(4) 1.2 amperes

16 The potential difference across R_3 is

- (1) 8.0 volts
(2) 24 volts
(3) 48 volts
(4) 72 volts

17 If the ratio of the current in R_3 to the current in R_2 is 4:5, the resistance of R_2 is

- (1) 5.0 ohms
(2) 8.0 ohms
(3) 24 ohms
(4) 60. ohms

18 The power supplied to the circuit is

- (1) 220 watts
(2) 190 watts
(3) 72 watts
(4) 24 watts