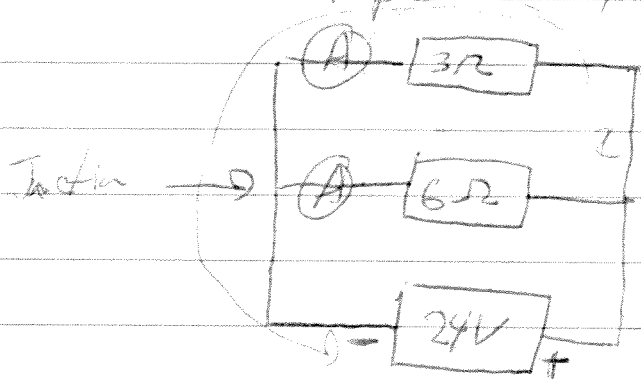


Parallel Circuit

Parallel Circuits have more than 1 current path.

Result: if part of the circuit is interrupted, the entire circuit may not fail. (Ex. Light bulb burns out at home)

Junction - Point at which current separates into more than 1 path.



- Each resistor comprised an indep. path

$$V_T = V_1 = V_2 = V_3$$

$$I_T = I_1 + I_2 + I_3$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Solve for I $\frac{V}{R} = \frac{IR}{R}$ $I_1 = \frac{V}{R} = \frac{24}{3\Omega} = 8A$

$$I_T = 8A + 4A = 12A$$

$$I_2 = \frac{V}{R} = \frac{24V}{6\Omega} = 4A$$

Solve for Resistance $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{3\Omega} + \frac{1}{6\Omega} = \frac{1}{2}$ $R_T = 2\Omega$
By cross, multiplied

Note: Overall resistance is less than resistance at any single point.

- When you add resistors, you are adding new paths,

Use highway example - Add more lanes, easier to get around

From $V=IR$ More highway choices $\uparrow$ Current
- + b

In Parallel Circuits
Add resistors

Overall
Resistance $\downarrow$
(Overall)


Overall
Current $\uparrow$

Ex 2

④ Find the current across each resist and the overall resistance

Add 70Ω Resistor

$$V_T = V_1 = V_2 = V_3 = 24V$$

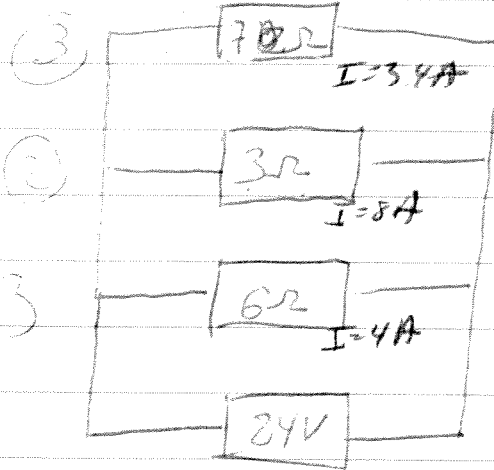


$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \frac{1}{R_T} = \frac{1}{6\Omega} + \frac{1}{3\Omega} + \frac{1}{70\Omega} = \frac{1}{1.5\Omega}$$

$$\frac{1}{R_T} = \frac{1}{0.6428} \quad (\text{by Calc}) \quad R_T = 0.6428 \approx \frac{9}{14} \quad 1.55\Omega$$

$$I_T = \frac{V_T}{R_T} = \frac{24V}{0.6428} = 37.33A$$

Parallel Circuits

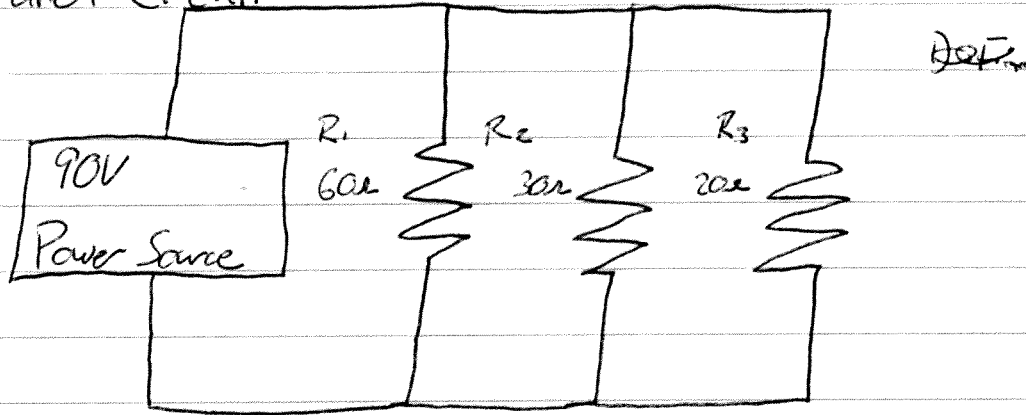

1) Find the equivalent Resistance of the circuit

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \quad \frac{1}{R_T} = \frac{1}{60\Omega} + \frac{1}{30\Omega} + \frac{1}{20\Omega}$$

$$\frac{1}{R_T} = \frac{6}{60\Omega} \quad R_T = 10\Omega$$

2) Find the Current in the entire Circuit

$$V_T = I_T R_T \quad I_T = \frac{V_T}{R_T} \quad I_T = \frac{90V}{10\Omega} = 9A$$

3) Find the current through each branch

$$I_1 = \frac{V}{R_1} = \frac{90V}{60\Omega} = 1.5A$$

$$I_2 = \frac{V}{R_2} = \frac{90V}{30\Omega} = 3A$$

$$I_3 = \frac{V}{R_3} = \frac{90V}{20\Omega} = 4.5A$$